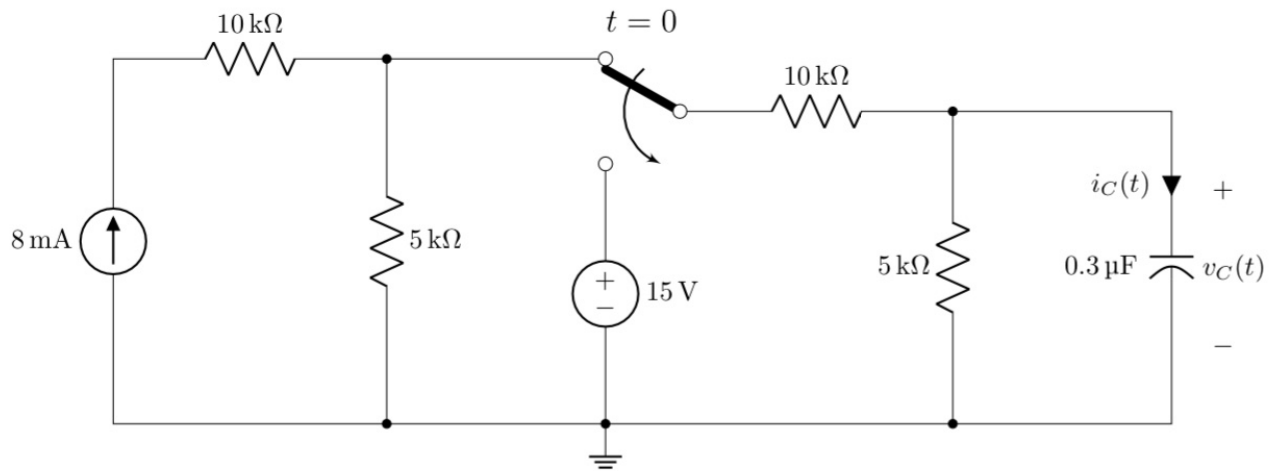


■ Question 1 of 4


[CO3] [16 marks]

The switch in the following circuit shifts at $t = 0$.




Analyze the Transient Behavior to answer the following questions–

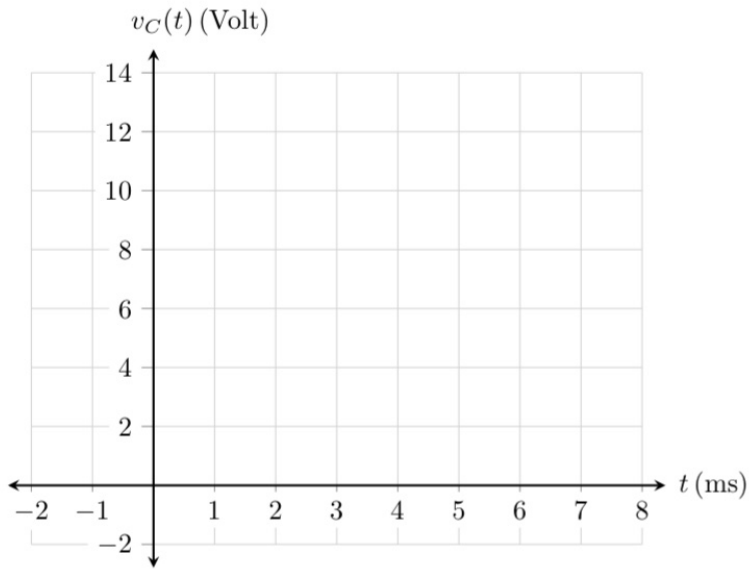- [10 marks] Determine the voltage response of the capacitor $v_C(t)$ as a function of time for $t > 0$.
- [3 marks] Determine the current $i_C(t)$ through the capacitor for $t > 0$.
- [3 marks] On the grids provided below, approximately draw the $v_C(t)$ and $i_C(t)$ found in (a) and (b) respectively.




Grid for $v_C(t)$

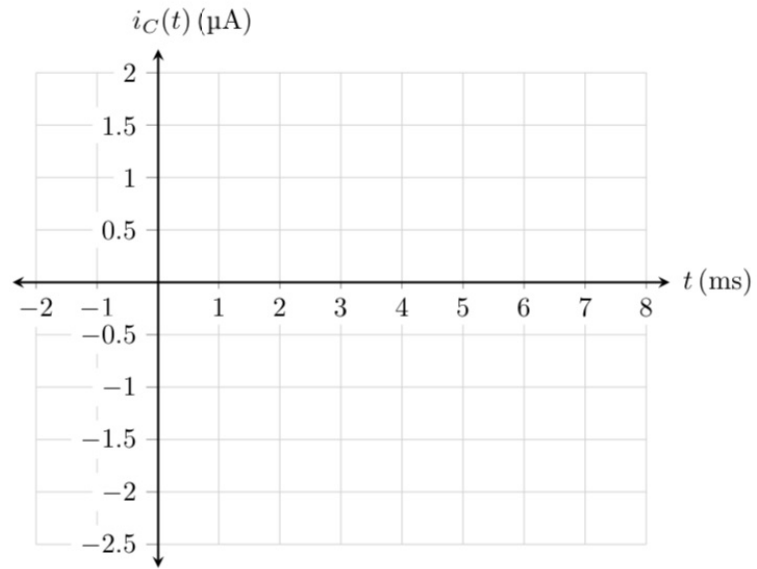

Grid for $i_C(t)$


(a) $t < 0$:

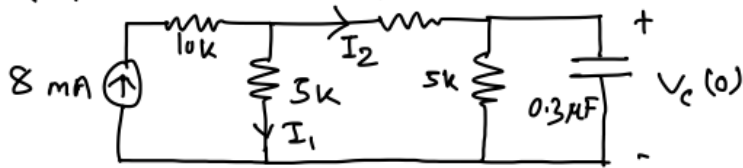

$$I_2 = 8 \times \frac{5}{5+10+5} = 2 \text{ mA}$$

$$\therefore V_c(0) = I_2 \times 5k = 10 \text{ V}$$

$t > 0$:

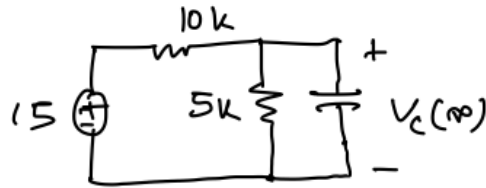

$$V_c(\infty) = 15 \times \frac{5}{10+5} = 5 \text{ V}$$

$$\tau = (10||5) \times 0.3\mu$$

$$= \frac{10}{3} \times 10^3 \times 0.3 \times 10^{-6}$$

$$= 1 \text{ ms}$$



$$\therefore V_c(t) = 5 + (10-5)e^{-t/\tau}$$

$$= 5 + 5e^{-1000t}$$

$$(b) i_c(t) = C \frac{d}{dt} V_c(t)$$

$$= (0 + (-1000) \times 5e^{-1000t}) \times 0.3 \times 10^{-6}$$

$$= -1.5e^{-1000t} \text{ mA}$$

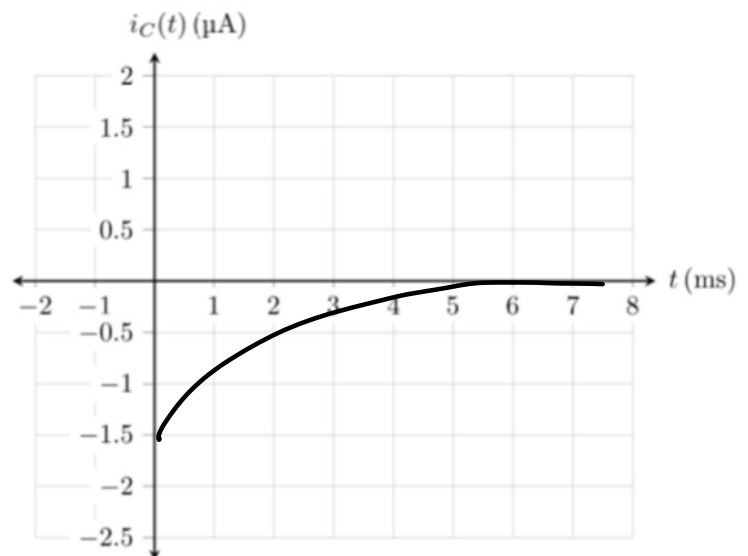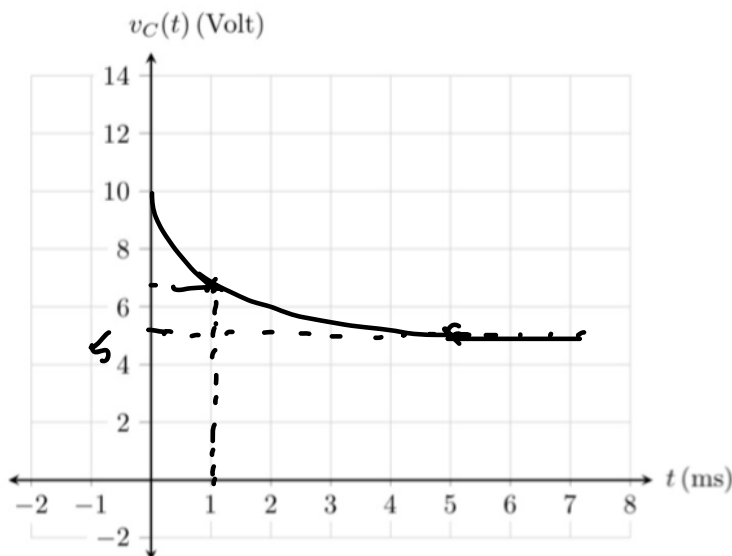

■ Question 2 of 4

[CO3] [10 marks]

When a voltage $V = 5\text{ V}$ is applied between terminals a and b of a linear two terminal circuit 'X', the circuit draws a current $I = 2\text{ A}$ as shown in *Figure 1* below. When the terminals are shorted, 3 A current flows as shown in *Figure 2*.

- [2 marks] Derive a relationship between I and V .
- [2 marks] Draw the relationship found in (a) on the grid provided below.
- [6 marks] If the circuit in *Figure 3* is an alternative version of the circuit 'X', determine the voltage V' and the resistance R' .

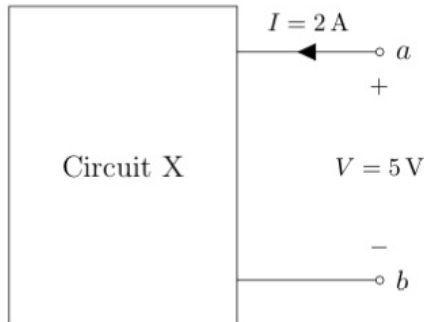


Figure 1

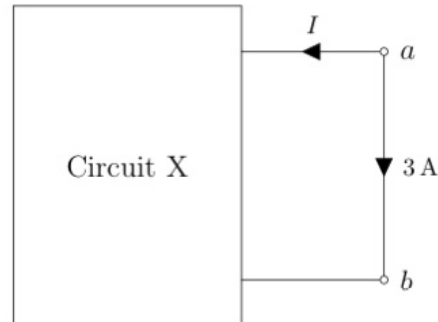


Figure 2


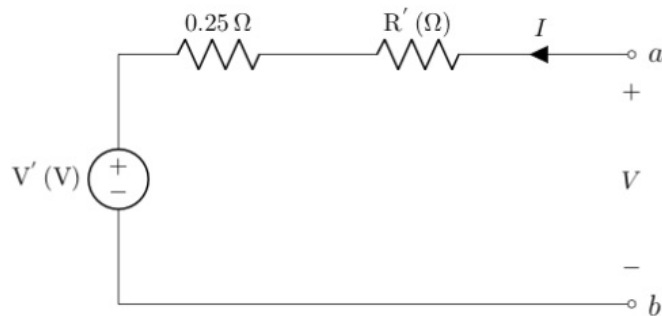



Figure 3

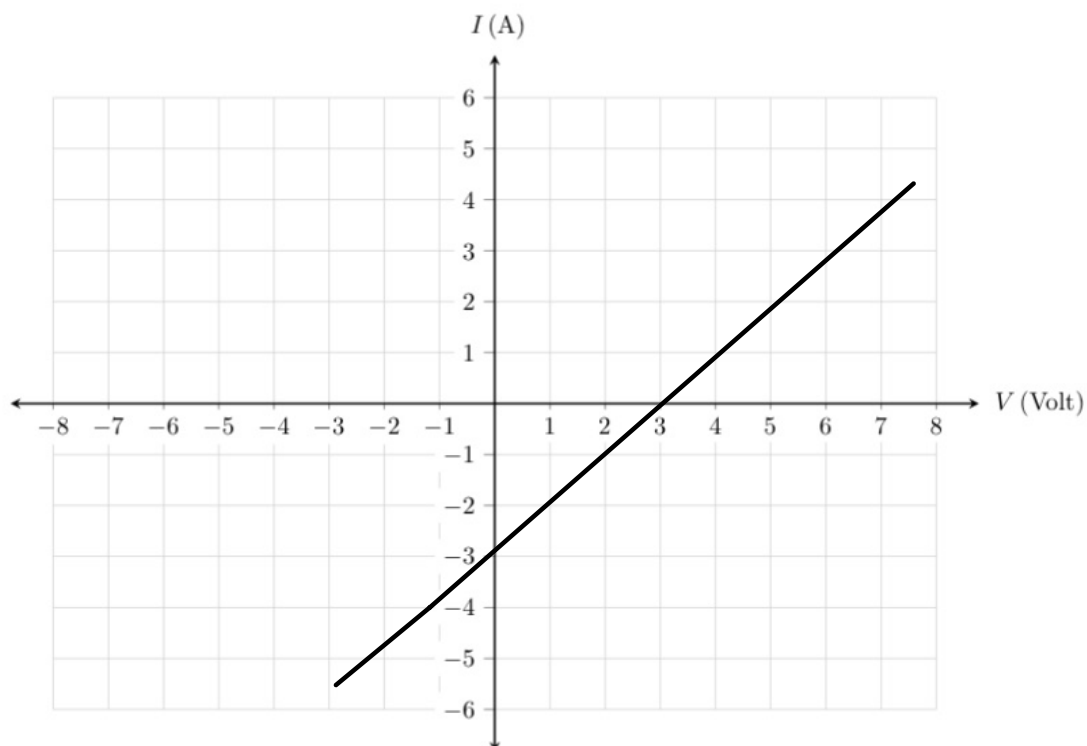

$S_x + \frac{18}{2} = 2$
 $(5, 2)$ $(0, 3)$
 $I = V - 3$
 $R' = 0.75$
 $V' = 3$

■ Question 3 of 4

[CO3] [16 marks]

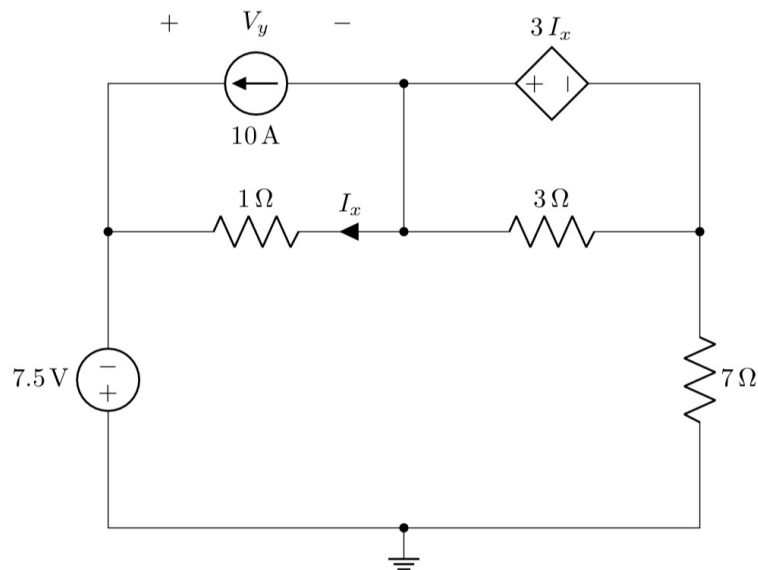


From the above circuit, answer the following questions-

- (a) [13 marks] Find V_y using **Superposition principle**.

After applying Superposition principle you may use any analysis technique you prefer (Nodal, Mesh, Src Tx etc.).

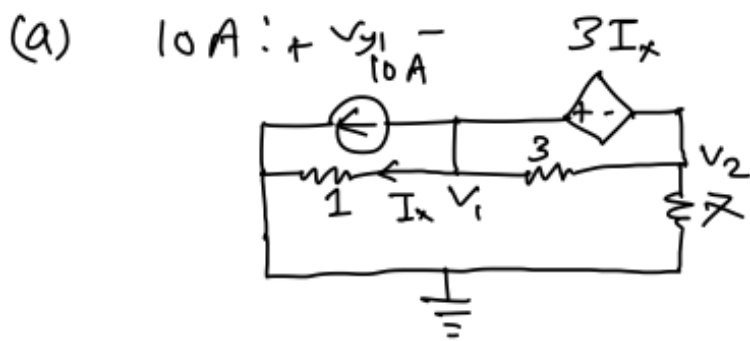- (b) [3 marks] Find the **power consumed/supplied** by the **current source** (with proper \pm sign and unit).



$$1 + 2: \quad V_1 - V_2 = 3 \times \frac{V_1}{1}$$


$$\Rightarrow -2V_1 - V_2 = 0$$

$$\text{Supermode: } V_1 + 10 + \frac{V_2}{2} = 0$$

$$\Rightarrow V_1 + \frac{V_2}{2} = -10$$

$$\therefore V_1 = -14, \quad V_2 = 28$$

$$\therefore v_{y1} = -V_1 = 14V$$

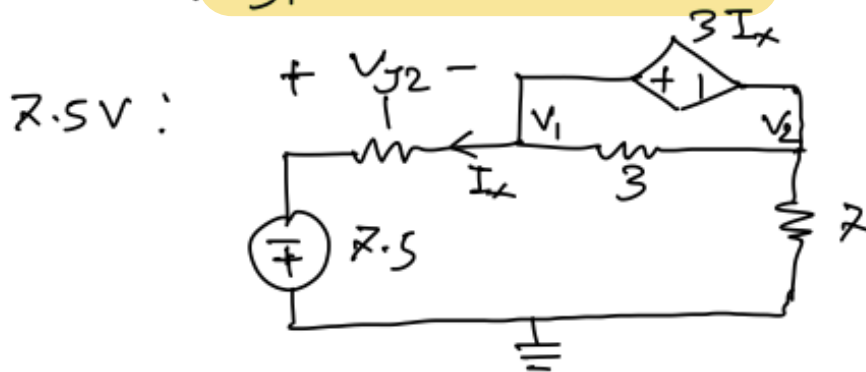

$$1 + 2: \quad V_1 - V_2 = 3 \times (V_1 + 2.5)$$

$$\Rightarrow -2V_1 - V_2 = 22.5$$

$$\text{Supermode: } \frac{V_1 + 2.5}{1} + \frac{V_2}{2} = 0$$

$$\Rightarrow V_1 + \frac{V_2}{2} = -2.5$$

$$V_1 = -6, \quad V_2 = -10.5$$

$$\therefore V_{y2} = -7.5 - v_1 = -1.5 \text{ V}$$


$$\therefore V_y = V_{y1} + V_{y2} = 14 - 1.5 = 12.5 \text{ V}$$

$$(b) P_{10A} = 10 \times V_y = -125 \text{ W} \quad \begin{matrix} \text{(supplying)} \\ \text{(consuming)} \end{matrix}$$

■ Question 4 of 4

[CO3] [8 marks]

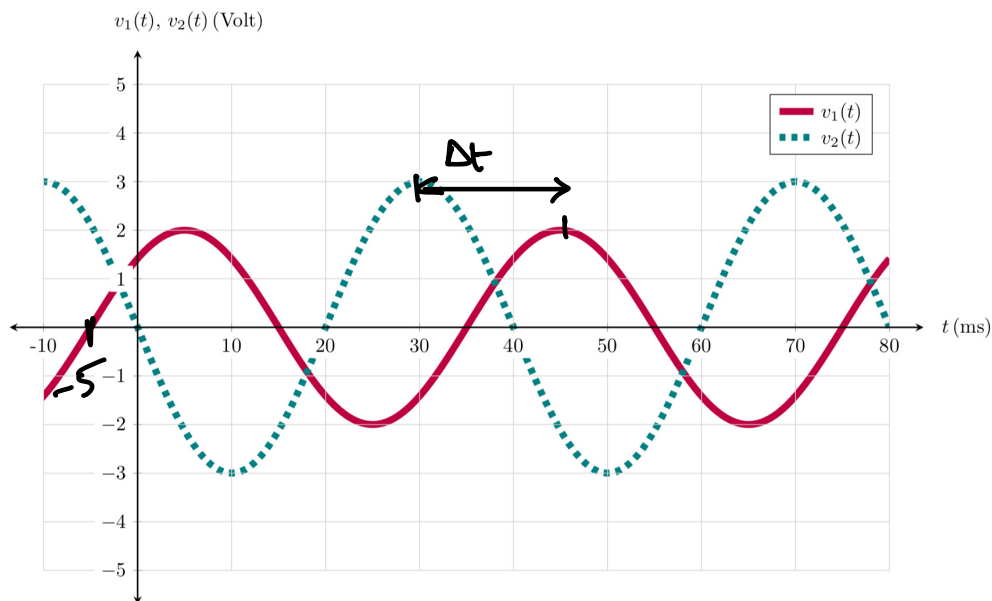Two ac voltage waveforms $v_1(t)$ and $v_2(t)$ from a circuit are plotted below as a function of time t .



(a) [4 marks] Determine the phase difference between the two and specify which one is leading.

(b) [4 marks] Write analytical expressions for both $v_1(t)$ and $v_2(t)$. From the expressions, verify the fact found in (a).

$$a) \Delta t = 45 - 30 = 15 \text{ ms}$$

$$T = 40 \text{ ms}$$

$$\omega = \frac{2\pi}{40} \text{ rad/ms}$$

$$\Delta \phi = \frac{2\pi}{40} \times 15 = \frac{3\pi}{4} \text{ rad}$$

$$v_2(t) \text{ leads } v_1(t) \text{ by } \frac{3\pi}{4} \text{ rad}$$

$$b) \quad \phi_1 = \frac{2\pi}{40} \times 5 = \frac{\pi}{4}$$

$$v_1(t) = 2 \sin\left(\frac{2\pi}{40}t + \frac{\pi}{4}\right)$$

$$\begin{aligned} v_2(t) &= -3 \sin\left(\frac{2\pi}{40}t\right) \\ &= 3 \sin\left(\frac{2\pi}{40}t + \pi\right) \end{aligned}$$

$$\Delta\phi = \pi - \frac{\pi}{4} = \frac{3\pi}{4}$$

$$v_2(t) \text{ leads } v_1(t) \text{ by } \frac{3\pi}{4} \text{ rad}$$