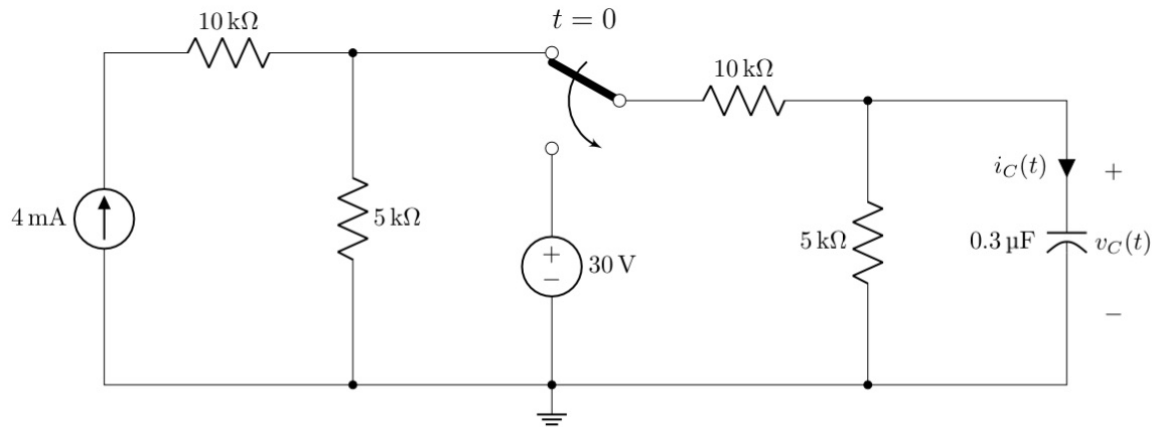


■ Question 1 of 4


[CO3] [16 marks]

The switch in the following circuit shifts at $t = 0$.




Analyze the Transient Behavior to answer the following questions–

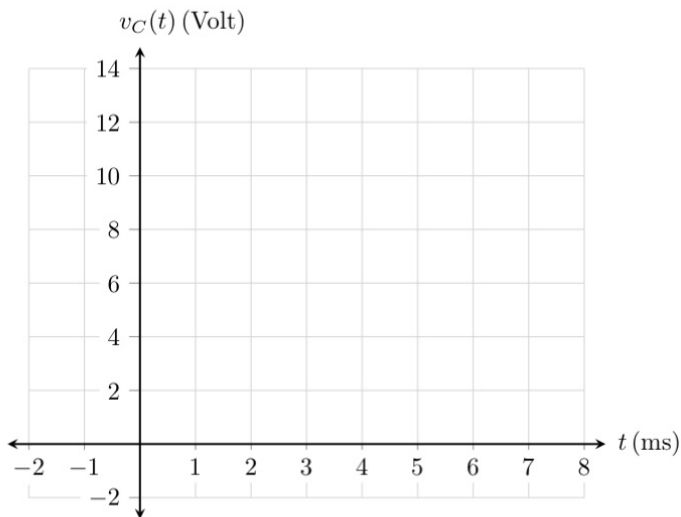- [10 marks] Determine the voltage response of the capacitor $v_C(t)$ as a function of time for $t > 0$.
- [3 marks] Determine the current $i_C(t)$ through the capacitor for $t > 0$.
- [3 marks] On the grids provided below, approximately draw the $v_C(t)$ and $i_C(t)$ found in (a) and (b) respectively.




Grid for $v_C(t)$

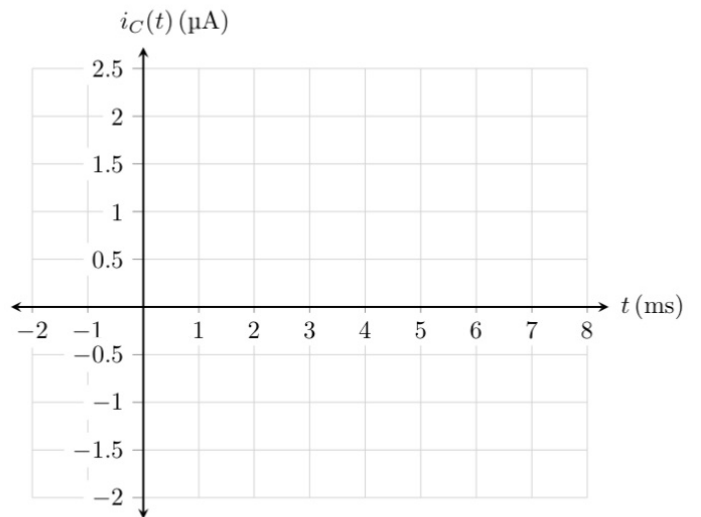

Grid for $i_C(t)$


(a) $t < 0$:

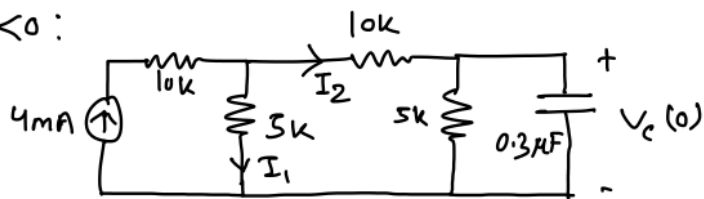

$$I_2 = 4 \times \frac{5}{5+10+5} = 1 \text{ mA}$$

$$\therefore V_c(0) = I_2 \times 5k = 5 \text{ V}$$

$t > 0$:

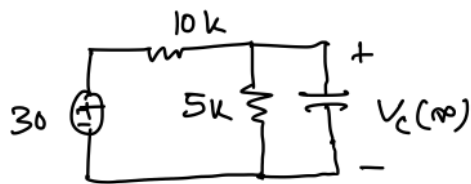



$$V_c(\infty) = 30 \times \frac{5}{10+5} = 10 \text{ V}$$

$$\begin{aligned} \tau &= (10||5) \times 0.3\mu \\ &= \frac{10}{3} \times 10^3 \times 0.3 \times 10^{-6} \\ &= 1 \text{ ms} \end{aligned}$$

$$\begin{aligned} \therefore V_c(t) &= 10 + (5-10)e^{-t/\tau} \\ &= 10 - 5e^{-1000t} \end{aligned}$$

$$(b) i_c(t) = C \frac{d}{dt} V_c(t)$$
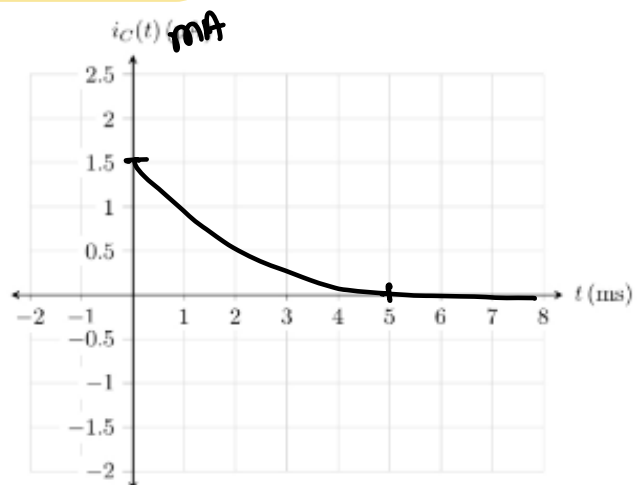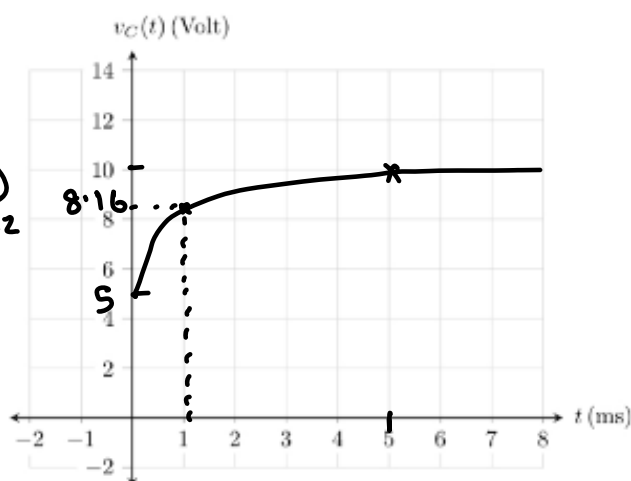
$$\begin{aligned} &= (0 - (-1000) \times 5e^{-1000t}) \times 0.3 \times 10^{-6} \\ &= 1.5e^{-1000t} \text{ mA} \end{aligned}$$



■ Question 2 of 4

[CO3] [10 marks]

When a voltage $V = 6\text{ V}$ is applied between terminals a and b of a linear two terminal circuit 'X', the circuit draws a current $I = 4\text{ A}$ as shown in *Figure 1* below. When the terminals are shorted, 2 A current flows as shown in *Figure 2*.

- [2 marks] Derive a relationship between I and V .
- [2 marks] Draw the relationship found in (a) on the grid provided below.
- [6 marks] If the circuit in *Figure 3* is an alternative version of the circuit 'X', determine the voltage V' and the resistance R' .

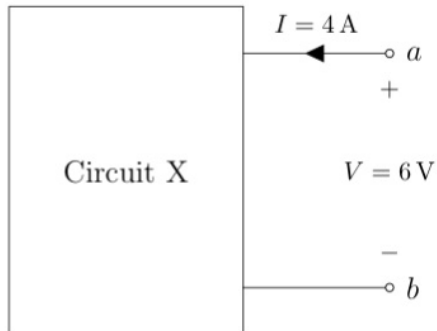


Figure 1

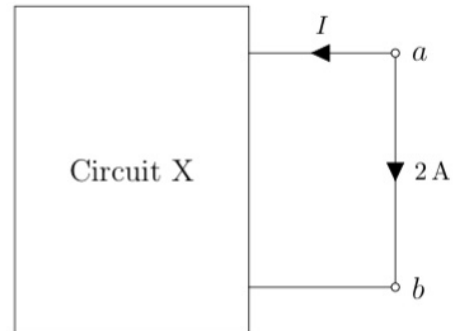


Figure 2


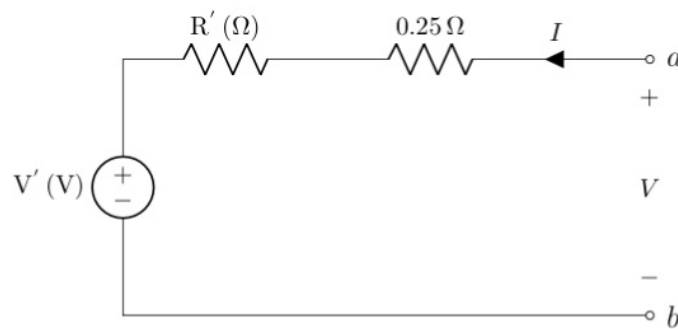


Figure 3

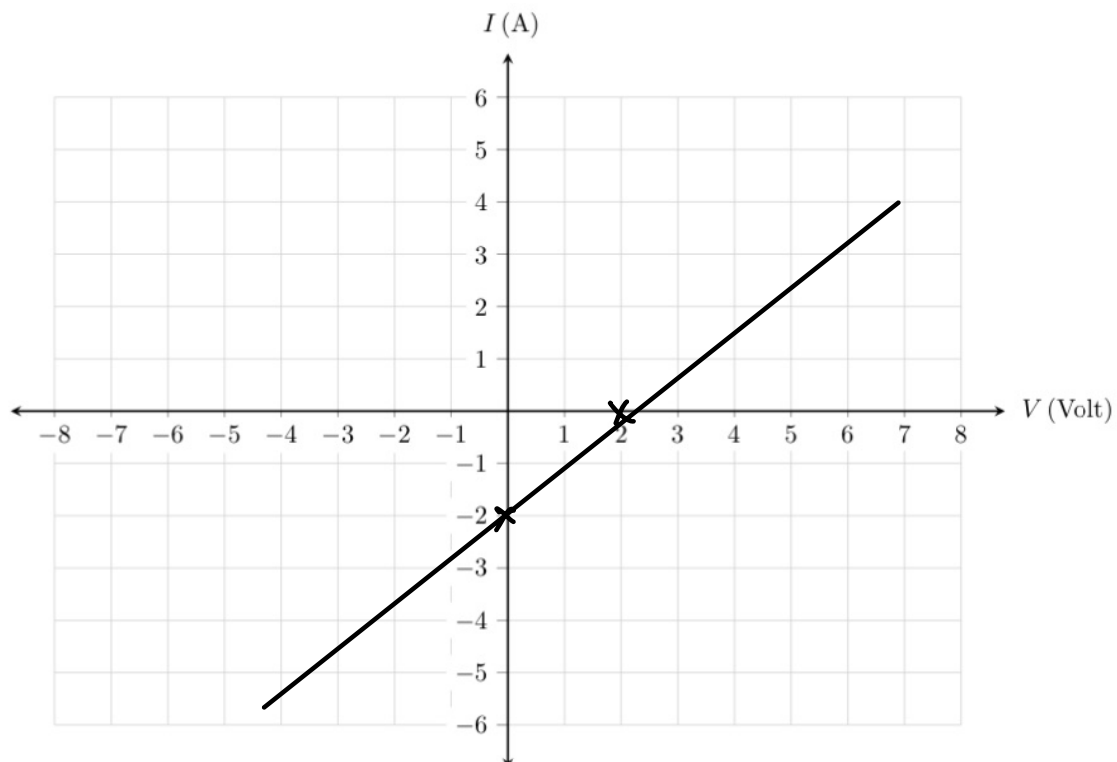

$\text{set } \underline{\underline{-A}}$
 $\underline{\underline{2}}$

$(6, 4)$ $(0, -2)$


$\text{eq} \rightarrow I = \cancel{4} V - 2$

$R' = 0.75$

$V' = 2$

■ Question 3 of 4

[CO2] [16 marks]

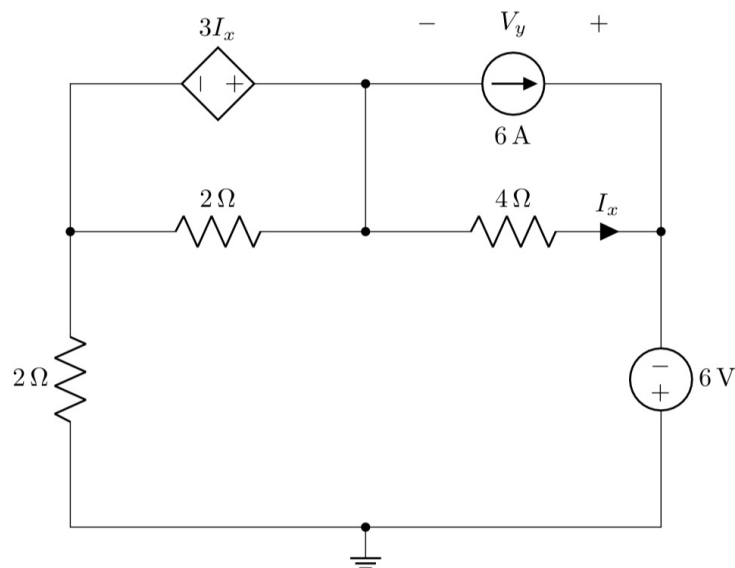


From the above circuit, answer the following questions-

- (a) [13 marks] Find V_y using **Superposition principle**.

After applying Superposition principle you may use any analysis technique you prefer (Nodal, Mesh, Src Tx etc.).

- (b) [3 marks] Find the **power consumed/supplied** by the **current source** (with proper \pm sign and unit).

(a) 6A:

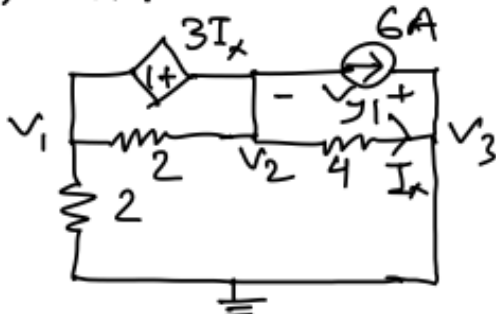

$$1+2: v_1 - v_2 = -3 \left(\frac{v_2 - v_3}{4} \right)$$

$$\Rightarrow v_1 + v_2 \left(-1 + \frac{3}{4} \right) - \frac{3}{4} v_3 = 0$$


$$\text{Supernode: } \frac{v_1}{2} + 6 + \frac{v_2 - v_3}{4} = 0$$

$$\Rightarrow \frac{v_1}{2} + \frac{v_2}{4} - \frac{v_3}{4} = -6$$

$$3: v_3 = 0$$

$$\therefore v_1 = -4, v_2 = -16$$

$$\therefore v_{y1} = v_3 - v_2 = 16V$$

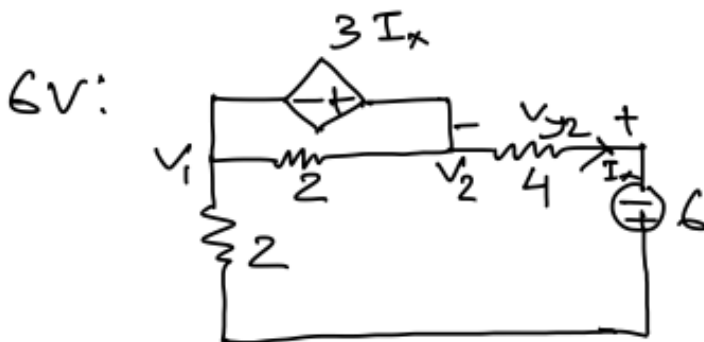

$$1+2: v_1 - v_2 = -3 \left(\frac{v_2 - (-6)}{4} \right)$$

$$\Rightarrow v_1 + v_2 \left(1 + \frac{3}{4} \right) = -\frac{18}{4}$$

$$\text{Super node: } \frac{v_1}{2} + \frac{v_2 + 6}{4} = 0$$

$$\Rightarrow \frac{v_1}{2} + \frac{v_2}{4} = -\frac{6}{4}$$

$$\therefore v_1 = -4, v_2 = 2$$

$$\therefore v_{y2} = -6 - v_2 = -8 \text{ V}$$

$$\therefore v_y = v_{y1} + v_{y2} = 16 - 8 = 8 \text{ V}$$


$$(b) P_{6A} = v_y \times 6 = 8 \times -6 = -48 \text{ W}$$

~~(consuming)~~ (supplying)

■ Question 4 of 4

[CO3] [8 marks]

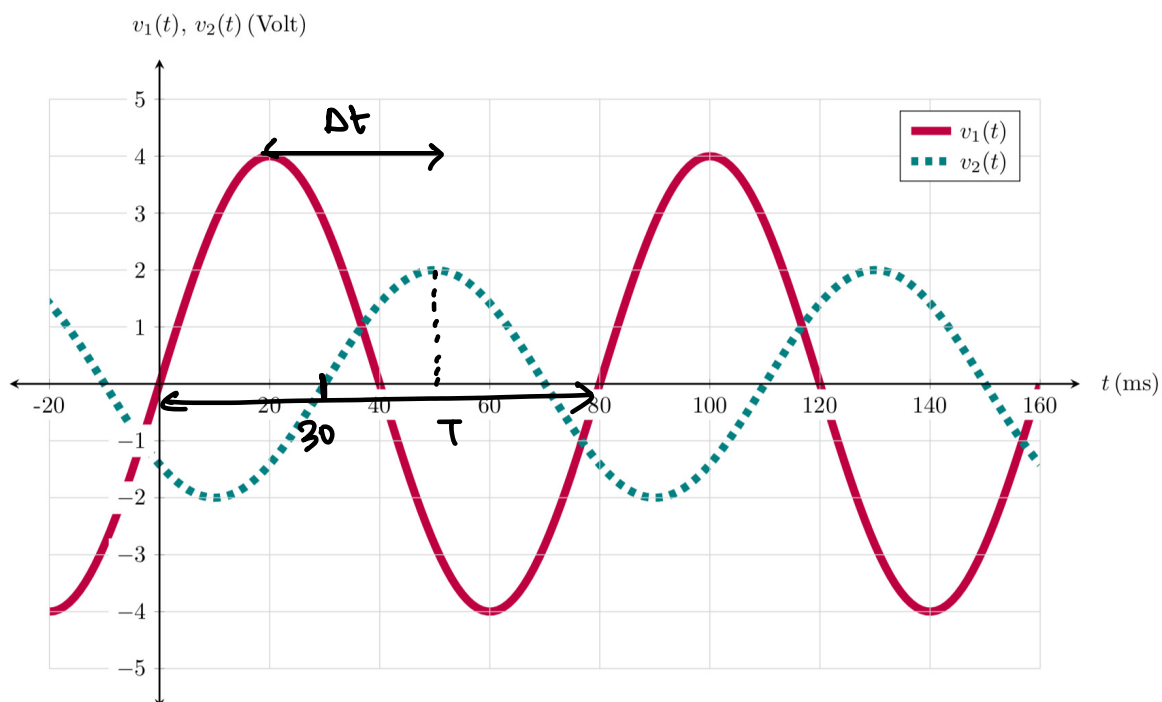Two ac voltage waveforms $v_1(t)$ and $v_2(t)$ from a circuit are plotted below as a function of time t .



(a) [4 marks] Determine the phase difference between the two and specify which one is leading.

(b) [4 marks] Write analytical expressions for both $v_1(t)$ and $v_2(t)$. From the expressions, verify the fact found in (a).

$$a) \Delta t = 50 - 20 = 30 \text{ ms}$$

$$T = 80 \text{ ms}$$

$$\omega = \frac{2\pi}{80} \text{ rad/ms}$$

$$\Delta\phi = \omega \times \Delta t = \frac{2\pi}{80} \times 30 = \frac{3\pi}{4} \text{ rad.}$$

$$v_1(t) \text{ leads } v_2(t) \text{ by } \frac{3\pi}{4} \text{ rad.}$$

$$b) v_1(t) = 4 \sin\left(\frac{2\pi}{80} t\right) \text{ V}$$

$$\phi_2 = 30 \text{ ms} \times \omega = 30 \times \frac{2\pi}{80} = \frac{3\pi}{4}$$

$$v_2(t) = 2 \sin\left(\frac{2\pi}{80} t - \frac{3\pi}{4}\right)$$

$$\text{phase diff} = 0 - \frac{3\pi}{4} = \frac{3\pi}{4}$$

$$v_1(t) \text{ leads } v_2(t) \text{ by } \frac{3\pi}{4} \text{ rad}$$