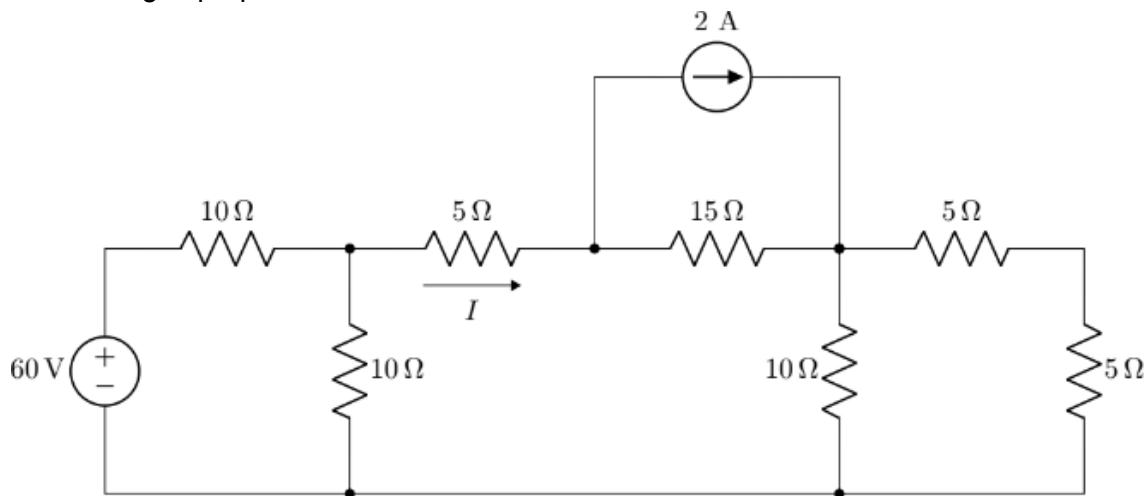


ASSIGNMENT-1

Superposition Theorem


Question 1:

Find I using superposition theorem.




Question 2:

Find I_o using superposition theorem.

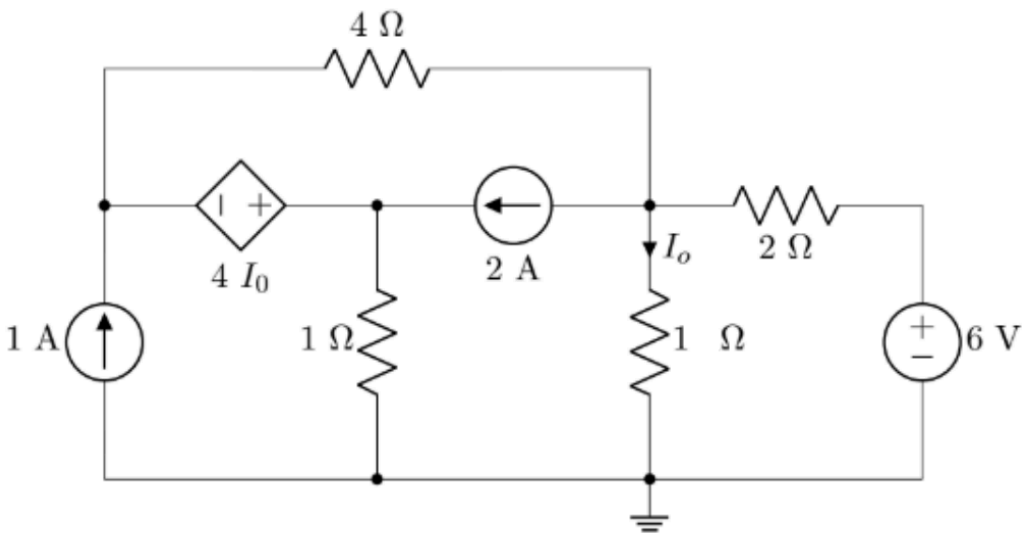


Question 3:

Find V_y using superposition theorem.

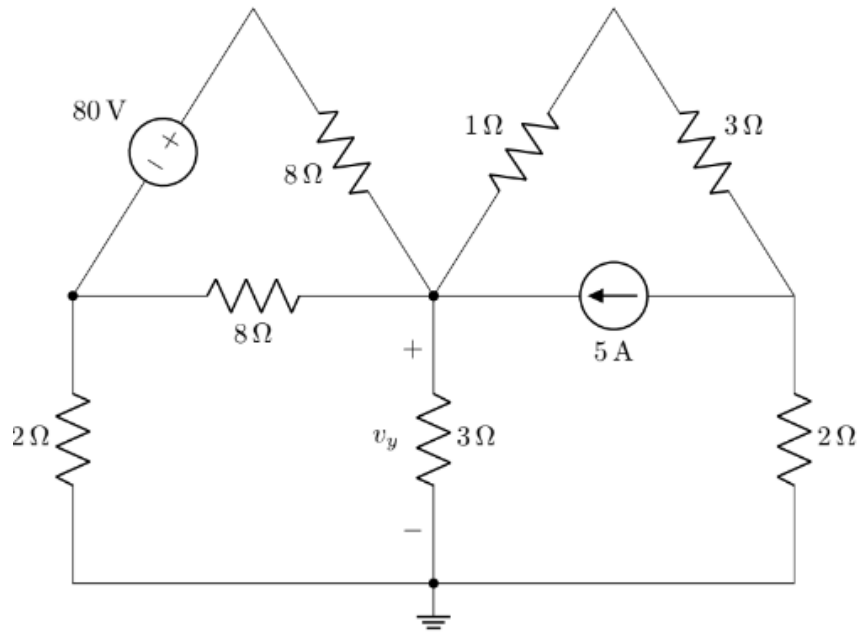


Question 4:

Find I_x using superposition theorem.

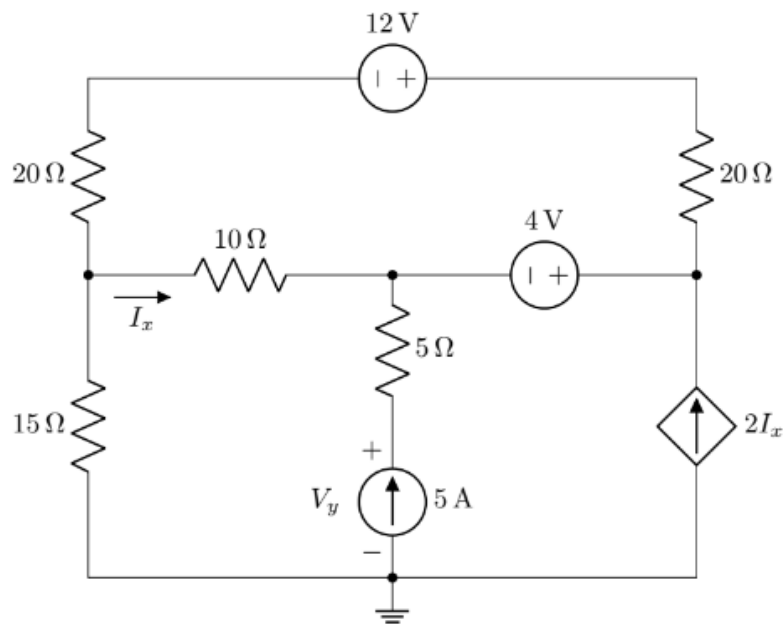

Question 5:

Find V_o using superposition theorem.

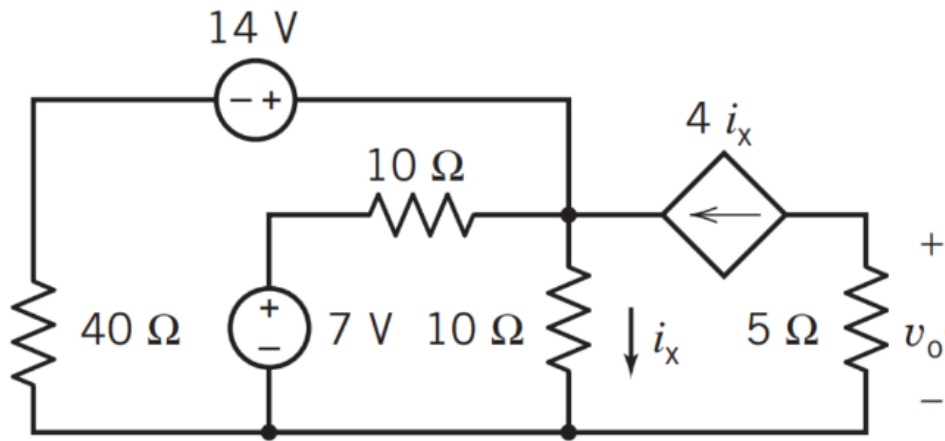**Question 6:**

Find V_o using superposition theorem.

