

# CSE250: Circuits and Electronics

## Spring 2023

### Practice Problems Set 3

## Thevenin's Theorem, Norton's Theorem, and Maximum Power Transfer Theorem



- 1.** Measurements made on terminals  $B - B'$  of a linear circuit in (a), which is known to be made up only of independent voltage sources and current sources, and resistors, yield the current-voltage characteristics shown in figure (b).

**Answer:**

$$V_{Th} = -3 \text{ V}$$

$$R_{Th} = \frac{3}{20} \text{ k}\Omega$$

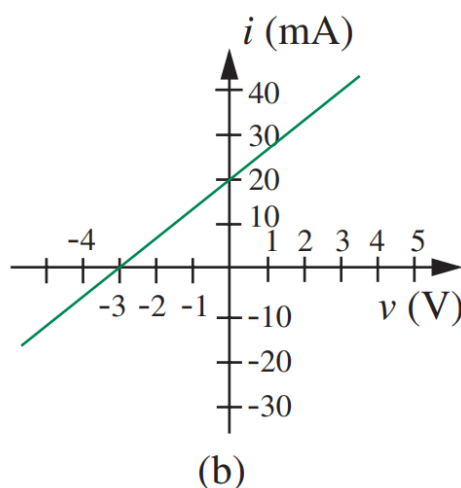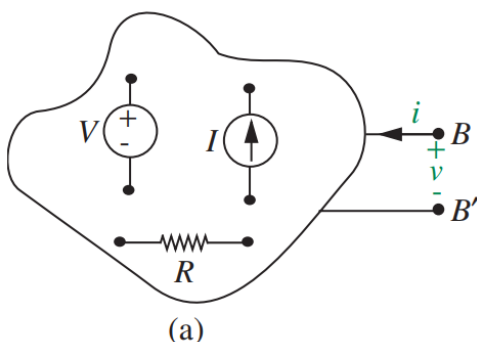Find the Thevenin equivalent of this circuit.




- 2.** Find the Thevenin equivalent circuit with respect to the terminals  $a, b$  for the circuit shown.


**Answer:**

$$V_{Th} = 64.8 \text{ V}$$

$$R_{Th} = 6 \Omega$$

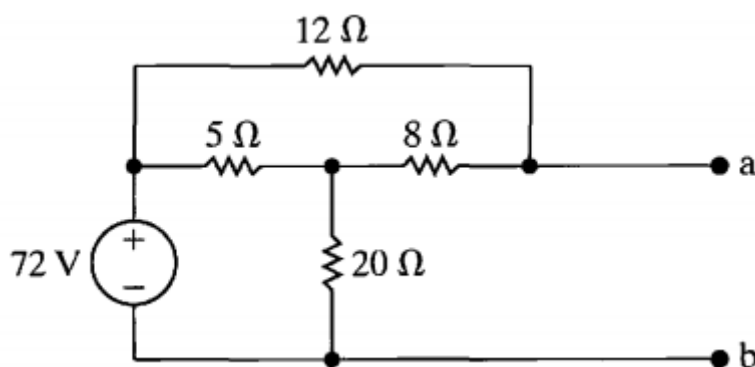

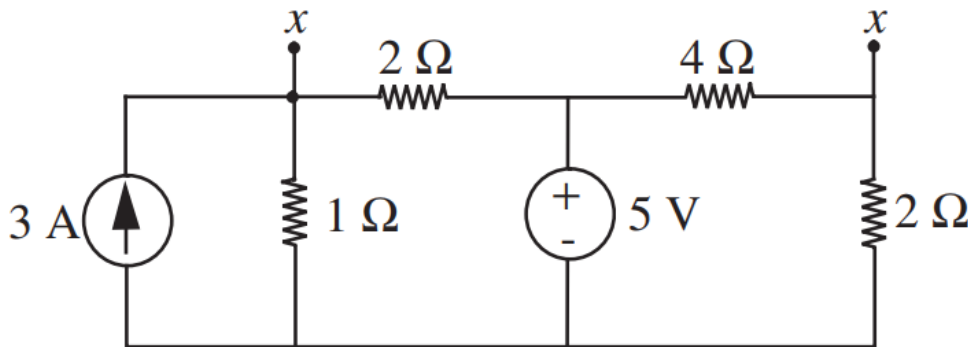3. Find the Norton equivalent at the terminals marked  $x - x$  in the circuit below.




**Answer:**

$$V_{Th} = 2 \text{ V}$$

$$R_{Th} = 2 \Omega$$

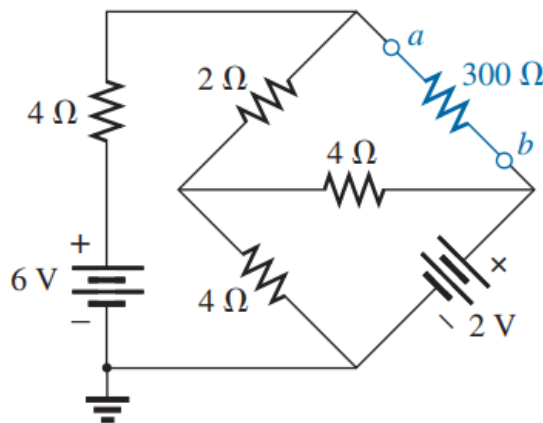4. For the network shown below, find the Thevenin equivalent circuit for the network external to the 300 Ω resistor.




**Answer:**

$$V_{Th} = 1.5 \text{ V}$$

$$R_{Th} = 2 \Omega$$

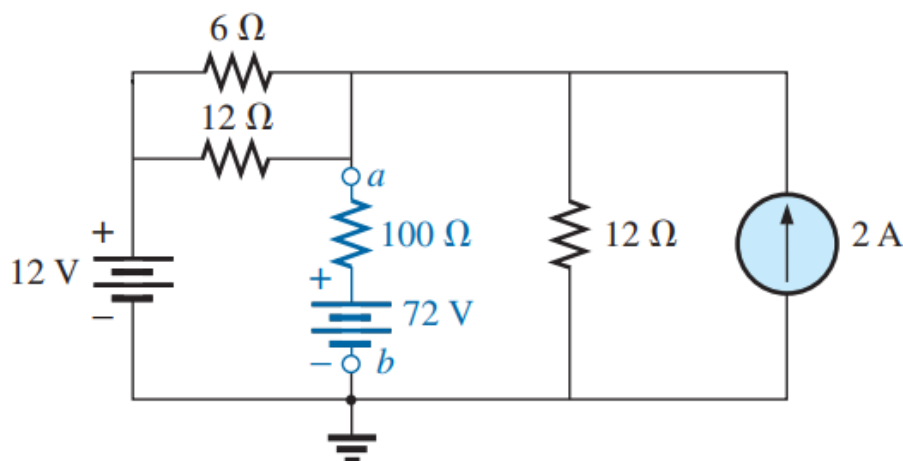- 5.
- Find the Norton equivalent circuit external to points  $a$  and  $b$ .
  - Find the magnitude and polarity of the voltage across the 100 Ω resistor using the results of part (a).




**Answer:**

$$I_N = 5 \text{ A}$$

$$R_{Th} = 3 \Omega$$

$$V_{100} = \mp 55.34 \text{ V}$$

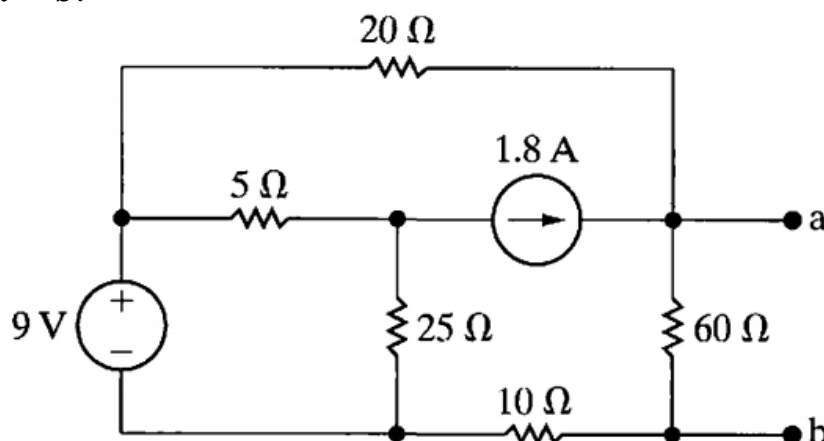6. Find the Thevenin equivalent with respect to the terminals  $a - b$ .




**Answer:**

$$V_{Th} = 30\text{ V}$$

$$R_{Th} = 20\ \Omega$$

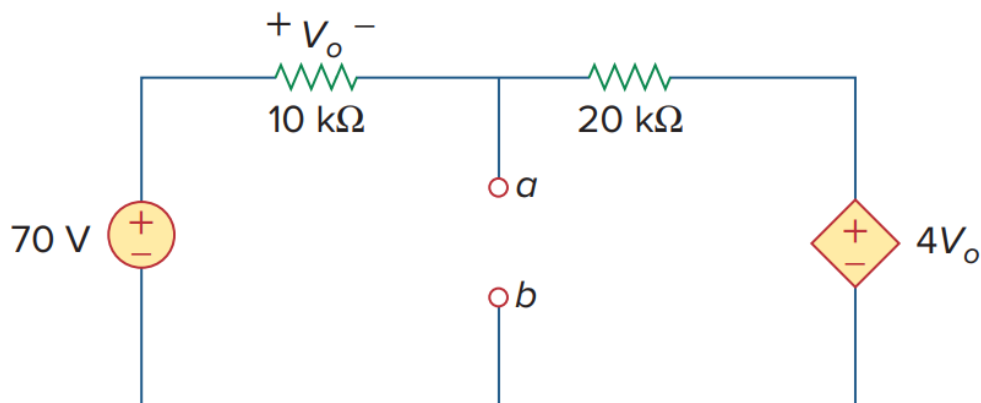7. Find the Thevenin equivalent at terminals  $a - b$  of the circuit shown below.




**Answer:**

$$V_{Th} = 60\text{ V}$$

$$R_{Th} = \frac{20}{7}\text{ k}\Omega$$

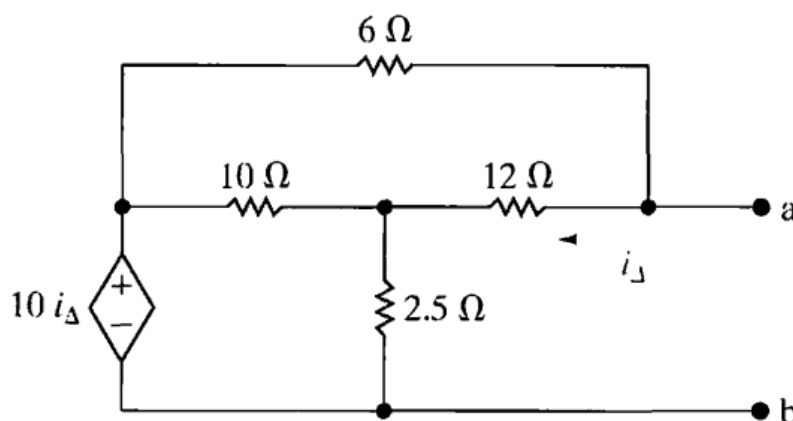8. Find the Thevenin equivalent with respect to the terminals  $a - b$ .




**Answer:**

$$V_{Th} = 0\text{ V}$$

$$R_{Th} = 8\ \Omega$$

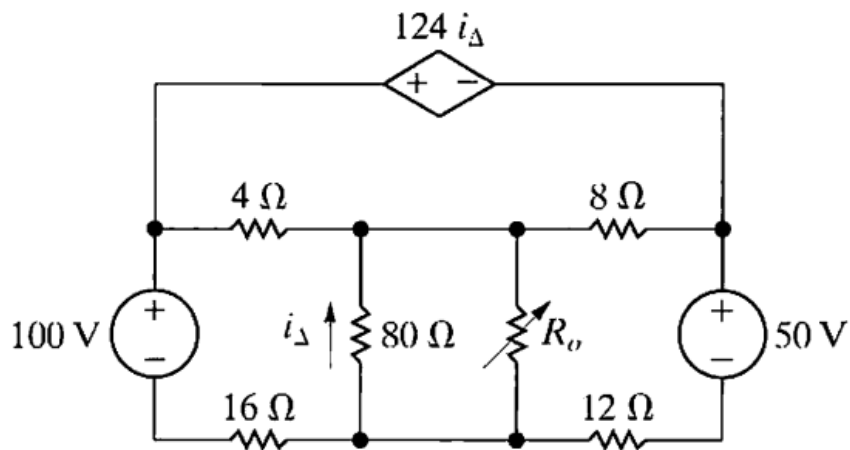9. The variable resistor ( $R_o$ ) is adjusted for maximum power transfer to  $R_o$ .

- Find the value of  $R_o$ .
- Find the maximum power that can be delivered to  $R_o$ .




**Answer:**

- $R_o = 6.4 \text{ k}\Omega$
- $P_{max} = 0.90 \text{ W}$

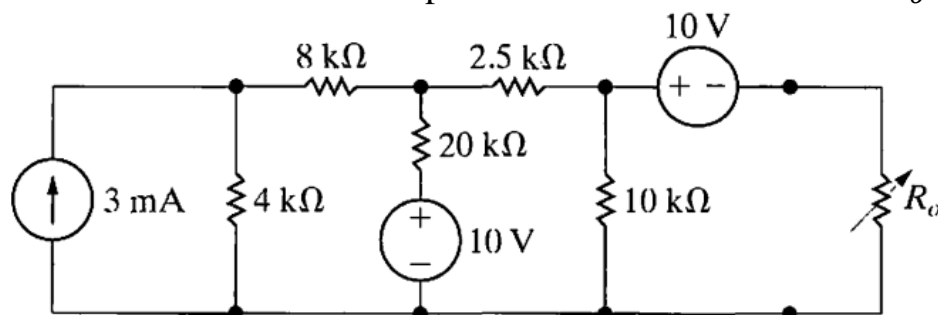10. The variable resistor ( $R_o$ ) is adjusted for maximum power transfer to  $R_o$ .

- Find the value of  $R_o$ .
- Find the maximum power that can be delivered to  $R_o$ .



**Answer:**

- $R_o = 5 \text{ k}\Omega$
- $P_{max} = 0.957 \text{ mW}$

**11.** Find the maximum power transferred to resistor  $R_L$ .

**Answer:**

$$R_L = -0.65 \text{ k}\Omega$$

$$P_{max} = \infty$$

(Theoretically)

